

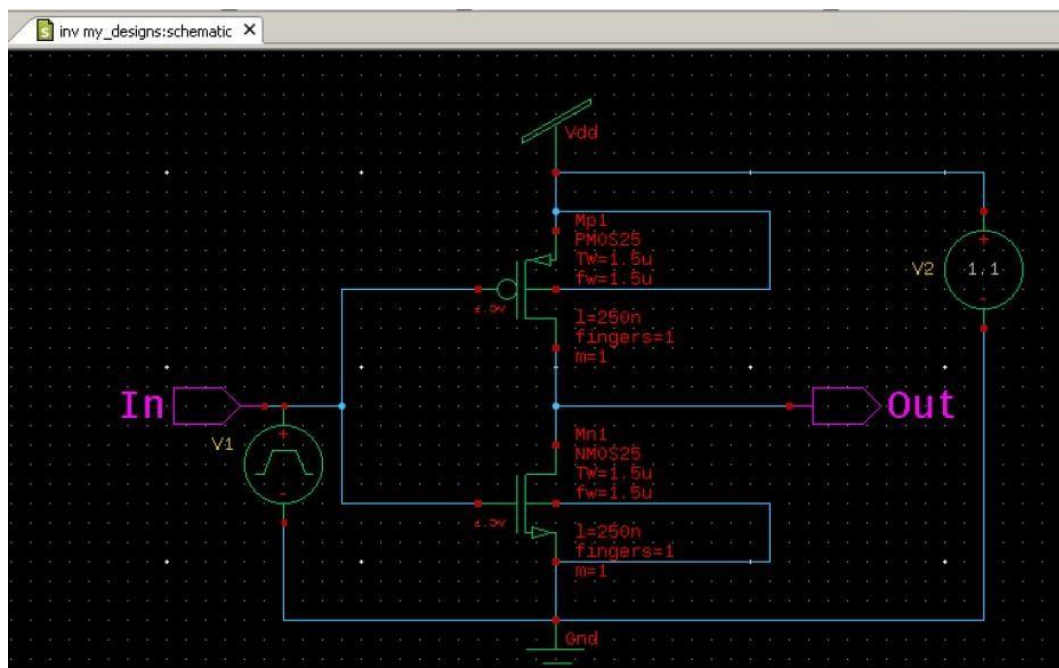


# CMOS INVERTER

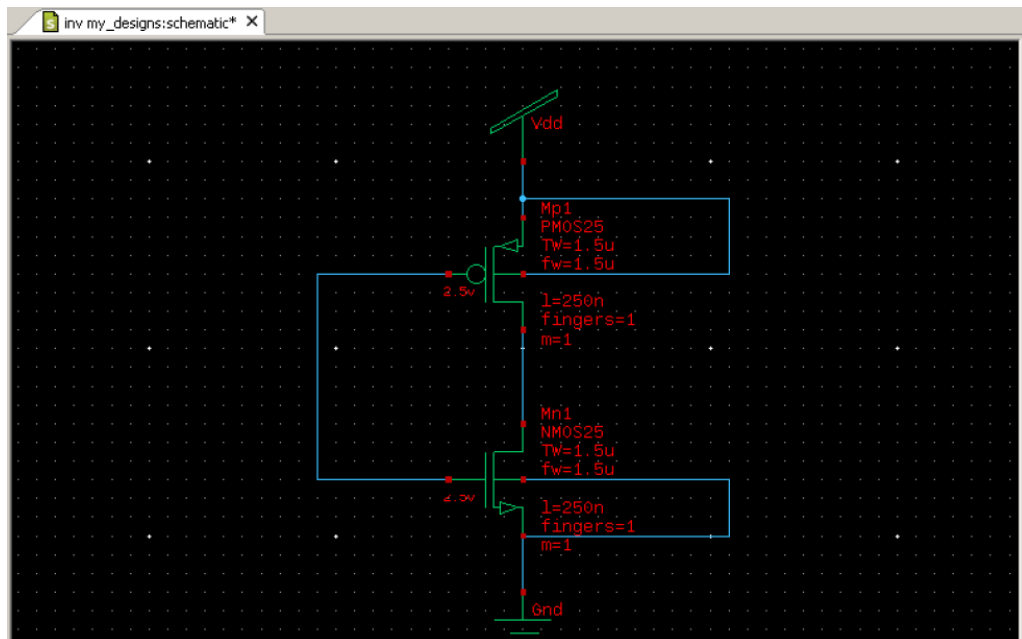

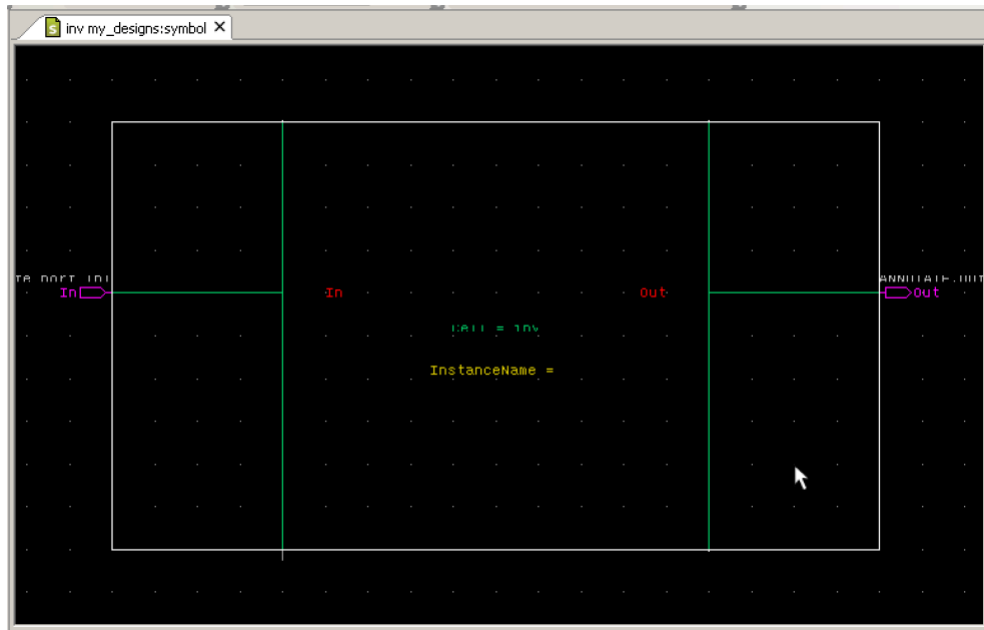

```

File Edit View Simulation Setup Window Help
[Icons] Concurrent 1 [Buttons]

* SPICE export by: S-Edit 2021.2.0
* Export time: Fri Nov 17 23:17:22 2023
* Design path: /home/wbpd007/SElisaR/VLSI_PD/Tanner_labs/Lab_01/CMOS_designs/lib.defs
* Library: my_designs
* Cell: inv
* Testbench: Spice
* View: schematic
* Export as: top-level cell
* Export mode: hierarchical
* Exclude empty: yes
* Exclude .model: no
* Exclude .hdl: no
* Exclude .end: no
* Exclude paths: yes
* Expand lines: no
* Exclude simulator commands: no
* Exclude global pins: no
* Exclude instance locations: no
* Control property name(s): SPICE


***** Simulation Settings - General Section *****
***** Top Level *****
NMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400 $h=600
Mmp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400 $h=600
V2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
V1 In Gnd PULSE(0 5 0 5n 5n 95n 200n) $ $x=3600 $y=3500 $w=400 $h=600

***** Simulation Settings - Analysis Section *****
.tran 10n 100n start=0n
.print tran v(out,Gnd) v(In,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****

.end

```

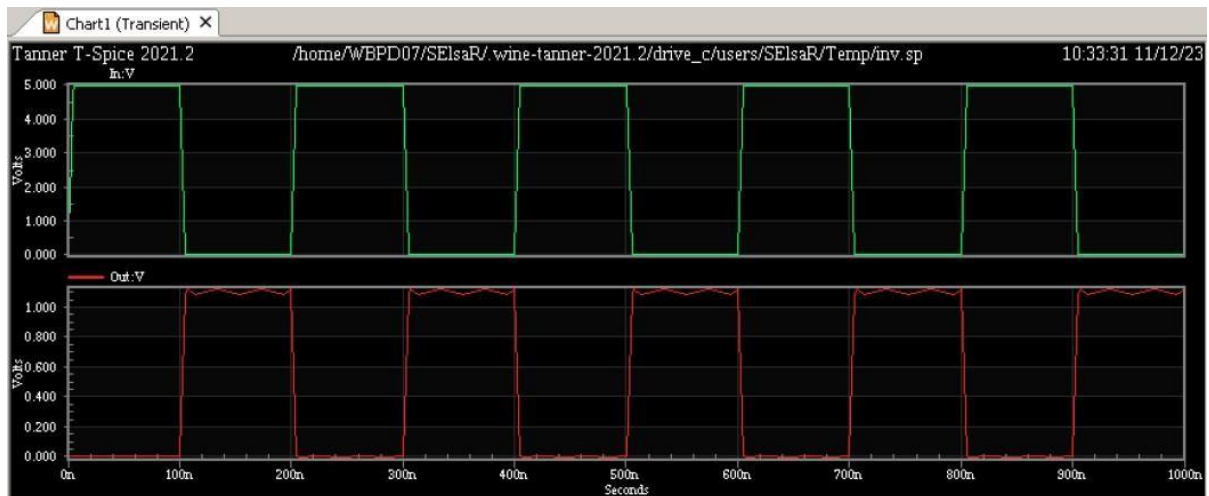

```

File Edit View Simulation Setup Window Help
Export mode: hierarchical
Exclude empty: yes
Exclude .model: no
Exclude .hdl: no
Exclude .end: no
Expand paths: yes
Wrap lines: no
Exclude simulator commands: no
Exclude global pins: no
Exclude instance locations: no
Control property name(s): SPICE


***** Simulation Settings - General Section *****
***** Top Level *****
MMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400 $h=600
MMp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400 $h=600
VV2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
*VV1 In Gnd PULSE(0 5 0 5n 5n 95n 200n) $ $x=3600 $y=3500 $w=400 $h=600

***** Simulation Settings - Analysis Section *****
VV1 In Gnd BIT ((101101110) pw=5n it=5n ht=5n on=1.1 off=0 rt=0.1n ft=0.1n delay=0)]
.tran 10n 100n start=0n
.print tran v(out,Gnd) v(In,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****


.end

```

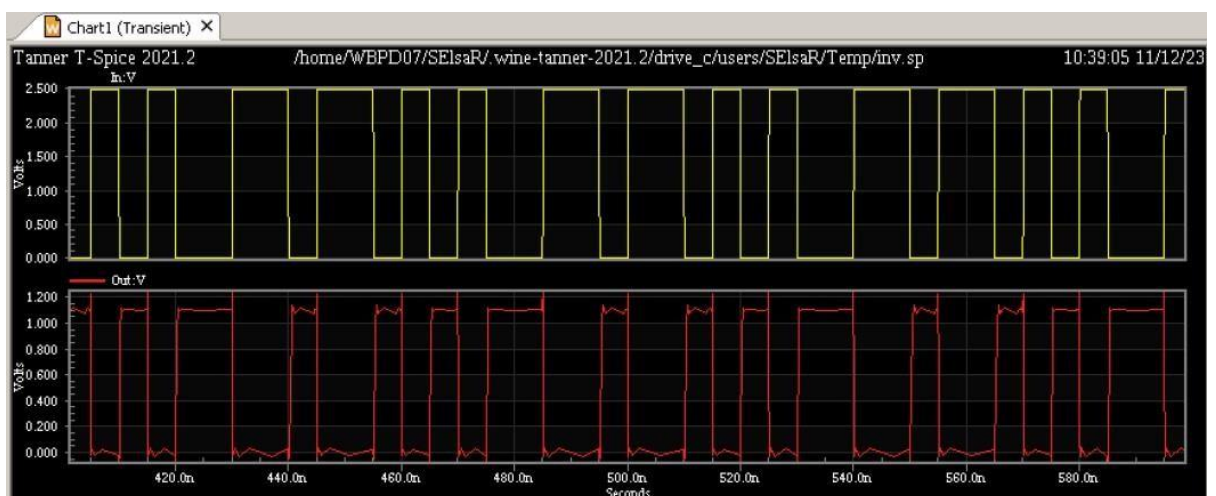



$$t_{PHL} = 0.3ns$$

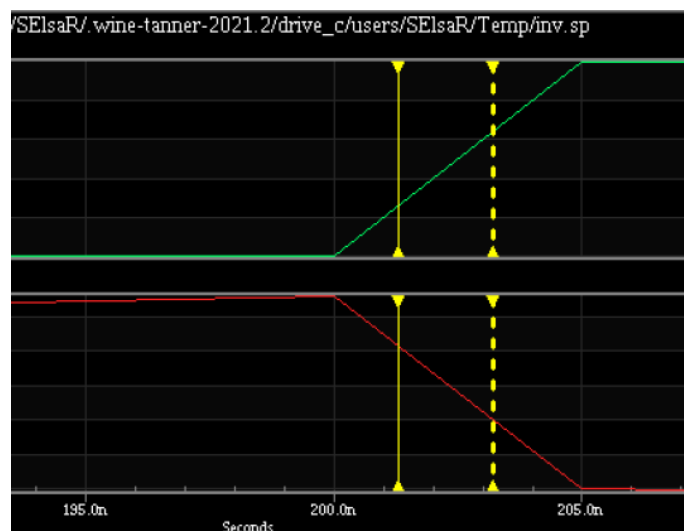

$$t_{PLH} = 0.2ns$$

$$t_P = (t_{PHL} + t_{PLH})/2$$

$$t_P = (0.3+0.2)/2 = 0.25ns$$

```
inv.sp
* Wrap lines: no
* Exclude simulator commands: no
* Exclude global pins: no
* Exclude instance locations: no
* Control property name(s): SPICE

***** Simulation Settings - General Section *****
MMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400
MMp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400
VV2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
VV1 In Gnd PULSE(0 5 0 5n 5n 95n 200n) $ $x=3600 $y=3500 $w=400 $h=600

***** Simulation Settings - Analysis Section *****
.power VV1 on 1000n
.tran 10n 1000n start=0n
.print tran v(Out,Gnd) v(In,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****

.end
```

Input file: inv.sp

Progress: Simulation completed

|                  |                    |                        |
|------------------|--------------------|------------------------|
| Total nodes: 8   | Active devices: 2  | Independent sources: 2 |
| Total devices: 4 | Passive devices: 0 | Controlled sources: 0  |

Model Definitions - 10

Computed Models - 2

Independent nodes - 5

Boundary nodes - 3

Total nodes - 8

Opening simulation database "/home/WBPD07/SElsar/.wine-tanner-2021.2/drive\_c/users/SElsar/Temp/inv.tsim"

Power Results

VV1 from time 0 to 1e-06

Average power consumed -> 2.243020e-06 watts

Max power 1.250016e-04 at time 5.1e-09

Min power 1.206684e-11 at time 0

```
inv.sp
* Exclude global pins: no
* Exclude instance locations: no
* Control property name(s): SPICE


***** Simulation Settings - General Section *****
***** Top Level *****
MMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400
MMp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400
VV2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
*VV1 In Gnd PULSE(0 5 0 5n 5n 95n 200n) $ $x=3600 $y=3500 $w=400 $h=600
VV1 In Gnd

***** Simulation Settings - Analysis Section *****
.step list temp 0 25 250 450

.dc lin source VV1 0 1.1 0.01
.print dc v(In,Gnd) v(Out,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****

.end
```

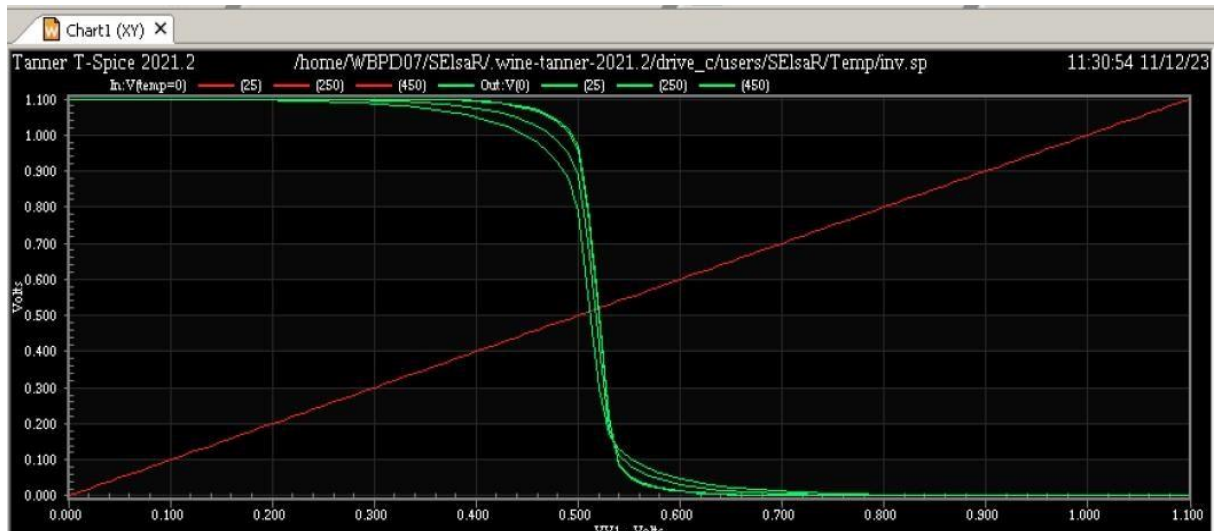

```

inv.sp *
* Wrap lines: no
* Exclude simulator commands: no
* Exclude global pins: no
* Exclude instance locations: no
* Control property name(s): SPICE


***** Simulation Settings - General Section *****
MMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400
MMp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400
V2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
V1 In Gnd

***** Simulation Settings - Analysis Section *****
.dc lin source VV1 0 1.1 0.1
.print dc v(out,Gnd) v(In,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****

.end

```

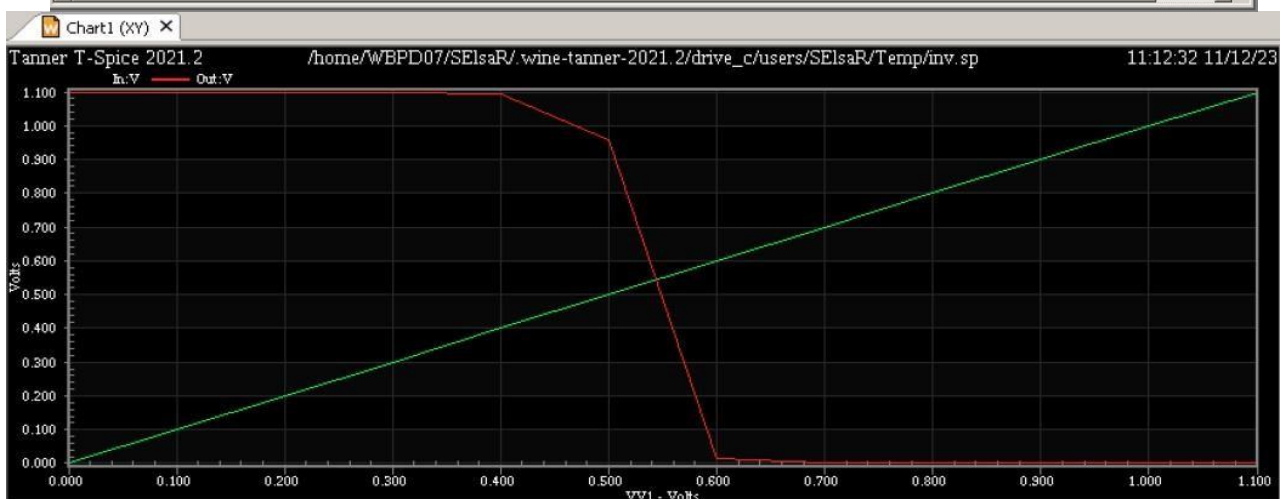



```
inv.sp *
* Exclude simulator commands: no
* Exclude global pins: no
* Exclude instance locations: no
* Control property name(s): SPICE

***** Simulation Settings - General Section *****
***** Simulation Settings - General Section *****
MMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400
MMp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400
VV2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
VV1 In Gnd PULSE(0 5 0 5n 5n 95n 200n) $ $x=3600 $y=3500 $w=400 $h=600

***** Simulation Settings - Analysis Section *****
.tf Out VV1
.tran 10n 1000n start=0n
.print tran v(Out,Gnd) v(In,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****

.end
```

File Edit View Simulation Setup Window Help

Input file: inv.sp  
Progress: Simulation completed

|                  |                    |                        |
|------------------|--------------------|------------------------|
| Total nodes: 8   | Active devices: 2  | Independent sources: 2 |
| Total devices: 4 | Passive devices: 0 | Controlled sources: 0  |

Computed Models - 2  
Independent nodes - 5  
Boundary nodes - 3  
Total nodes - 8

Opening simulation database "/home/WBPD07/SElsaR/.wine-tanner-2021.2/drive\_c/users/SElsaR/Temp/inv.tsim"

SMALL-SIGNAL TRANSFER FUNCTION: temperature=25.0

Out / VV1 = -8.0053e+05

Input resistance at VV1 = -inf  
Output resistance at Out = 4.5963e+03

|                   |              |
|-------------------|--------------|
| Parsing           | 0.24 seconds |
| Setup             | 0.04 seconds |
| Transfer function | 0.07 seconds |
| DC Analysis       | 0.02 seconds |
| Overhead          | 0.30 seconds |
| -----             |              |
| Total             | 0.69 seconds |

Simulation completed

```
inv.sp
***** Simulation Settings - General Section *****
***** Simulation Settings - General Section *****
MMn1 Out In Gnd Gnd NMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=3300 $w=400
Mmp1 Out In Vdd Vdd PMOS25 w=1.5u l=250n m=1 ad=975f pd=4.3u as=975f ps=4.3u nrd=433.33333m nrs=433.33333m $ $x=4800 $y=4400 $w=400
VW2 Vdd Gnd DC 1.1 $ $x=7200 $y=4500 $w=400 $h=600
^VW1 In Gnd PULSE(0 5 0 5n 5n 95n 200n) $ $x=3600 $y=3500 $w=400 $h=600
VW1 In Gnd

***** Simulation Settings - Analysis Section *****
.param wn=1.5u
.step lin param wn 0.5u 4.5u 1.0u
.dc lin source VW1 0 1.1 0.01
.print dc v(out,Gnd) v(in,Gnd)
.lib "/home/cad/eda/Tanner_2021/tanner-2021-2-rhel6-64/share/examples/Process/Generic_250nm/Models/Generic_250nm.lib" TT

***** Simulation Settings - Additional SPICE Commands *****

.end
```

